

Chapter3: Multiplexer, Latch, Buffer

Asst.Prof.Dr.Supakit Nootyaskool



Objective


- Describe concept multiplexer and de-multiplexer circuit.
- Compare and contrast latch circuit and buffer circuit.
- Explain truth table of set-reset flipflop.

Topic

- Multiplexer circuit
- Demultiplexer circuit
- Latch circuit
- Buffer circuit
- Set-Reset Flipflop



MULTIPLEXER CIRCUIT

Selector switch

 

Selector switch is mechanical switch for selecting the signal channels
We found the selector switch in electrical machines, radio event if the car.

Switch -> Multiplexer (MUX)

  

LazGlobal CD74HC4067 16-Channel Analog Digital Multiplexer Breakout Board Module For Arduino

★★★★★ 1 คะแนน


แบรนด์: No Brand |

฿36.00


฿50.00 -28%

โปรโมชั่น



จำนวน

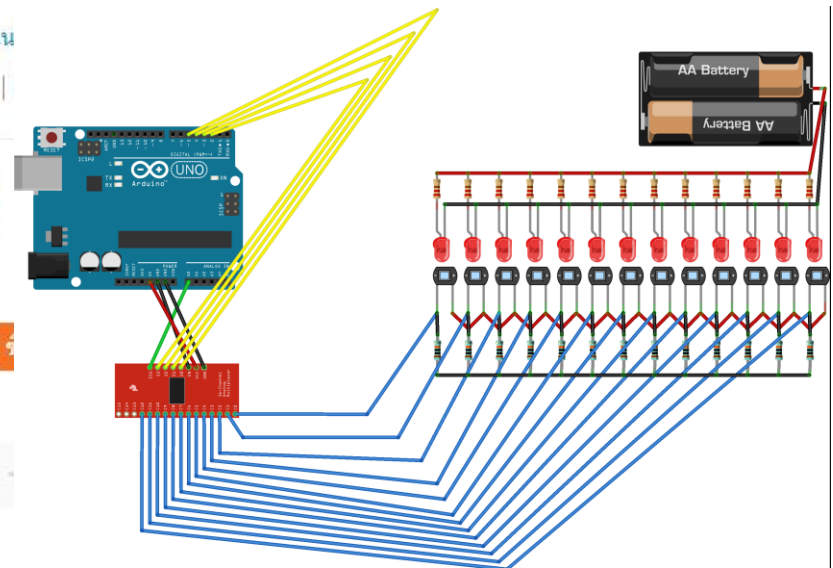


Compare between No MUX and MUX

 


What is circuit inside MUX and DEMUX

  

Multiplexer circuit

 


Multiplexer circuit

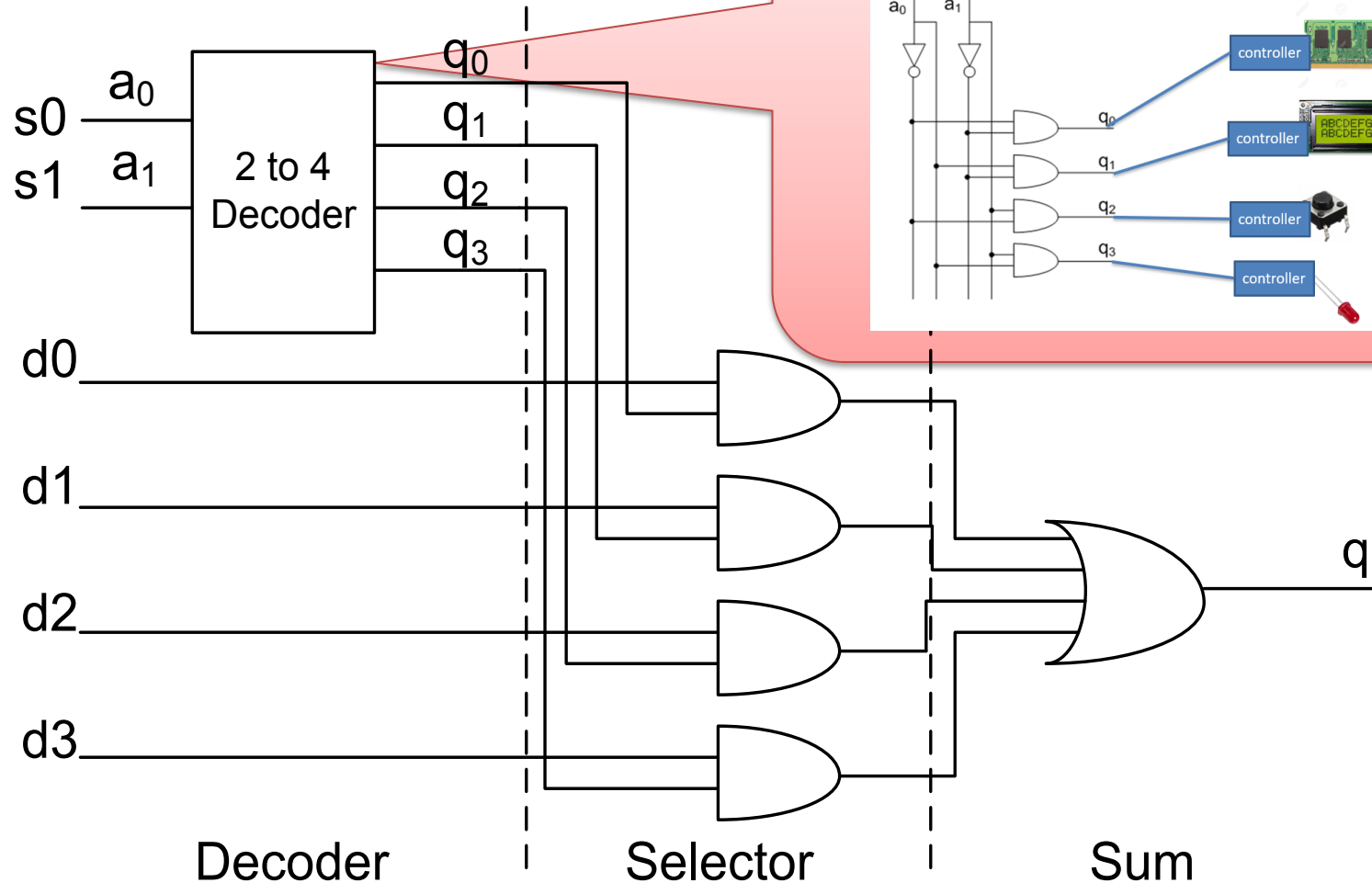


DEMULTIPLEXER CIRCUIT

De-multiplexer circuit

 

MUX + DEMUX

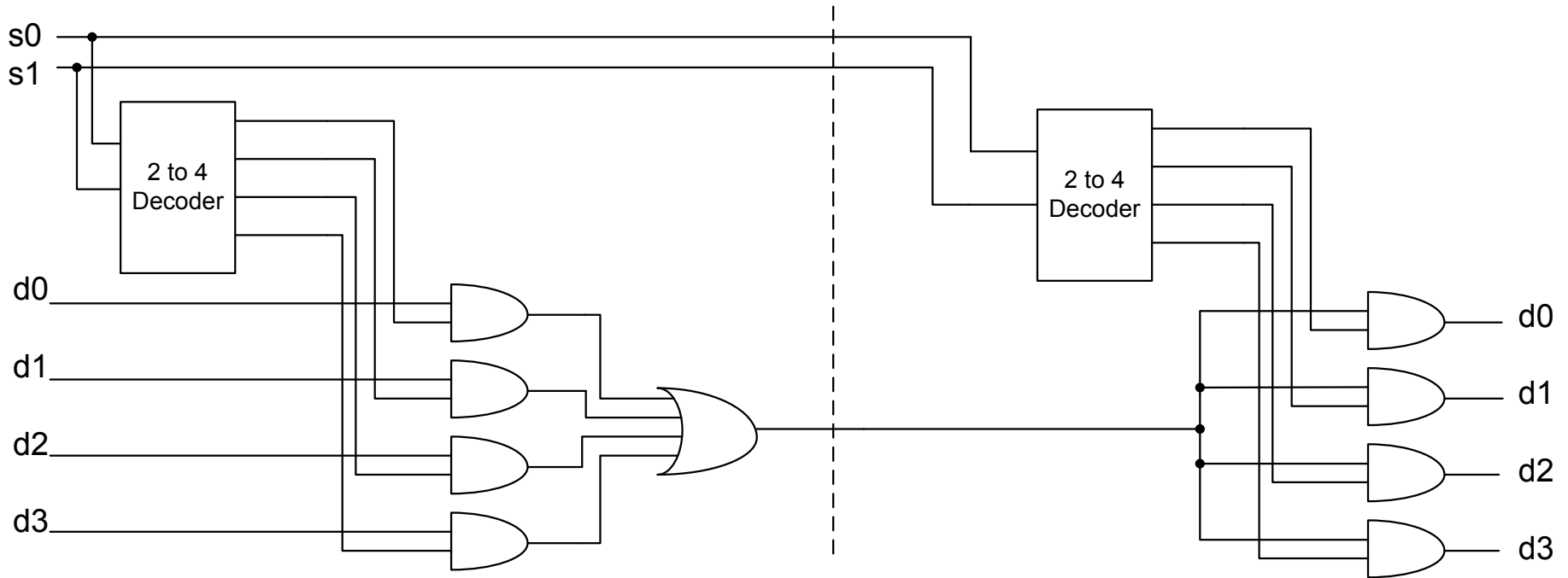


Example devices use MUX/DMUX




TRISTATE GATE

Tristate gate

 - Tristate gate is three logic levels (H/L/Z)
- High impendence (Z) means two junction having high resistance over $1\text{M}\Omega$ like open circuit.
- Tristate gate is applied to an output selector from two or more circuit.



| Enable | Input | Output |
|--------|-------|--------|
| 0 | 0 | Hi-Z |
| 0 | 1 | Hi-Z |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

 

Tristate gate datasheet and package

3CE32231 - APRIL 1999 - REVISED OCTOBER 2014

SN74LVC1G125 Single Bus Buffer Gate With 3-State Output

1 Features

- Available in the Ultra Small 0.64-mm² Package (DPW) With 0.5-mm Pitch
- Supports 5-V V_{CC} Operation
- Inputs Accept Voltages to 5.5 V
- Provides Down Translation to V_{CC}
- Max t_{pd} of 3.7 ns at 3.3 V
- Low Power Consumption, 10- μ A Max I_{CC}
- ± 24 -mA Output Drive at 3.3 V
- I_{off} Supports Live Insertion, Partial-Power-Down Mode, and Back-Drive Protection
- Latch-Up Performance Exceeds 100 mA Per JESD 78, Class II
- ESD Protection Exceeds JESD 22
 - 2000-V Human-Body Model (A114-A)
 - 200-V Machine Model (A115-A)
 - 1000-V Charged-Device Model (C101)

2 Applications

- Cable Modem Termination System
- High-Speed Data Acquisition and Generation
- Military: Radar and Sonar
- Motor Control: High-Voltage
- Power Line Communication Modem
- SSD: Internal or External
- Video Broadcasting and Infrastructure: Scalable Platform
- Video Broadcasting: IP-Based Multi-Format Transcoder
- Video Communications System

3 Description

This bus buffer gate is designed for 1.65-V to 5.5-V V_{CC} operation.

The SN74LVC1G125 device is a single line driver with a 3-state output. The output is disabled when the output-enable (OE) input is high.

The CMOS device has high output drive while maintaining low static power dissipation over a broad V_{CC} operating range.



The SN74LVC1G125 device is available in a variety of packages including the ultra-small DPW package with a body size of 0.8 mm \times 0.8 mm.

Device Information⁽¹⁾

| DEVICE NAME | PACKAGE | BODY SIZE (NOM) |
|--------------|------------|--------------------------|
| SN74LVC1G125 | SOT-23 (5) | 2.90 mm \times 1.60 mm |
| | SC70 (5) | 2.00 mm \times 1.25 mm |
| | SON (6) | 1.45 mm \times 1.00 mm |
| | DSBGA (5) | 1.40 mm \times 0.90 mm |
| | X2SON (4) | 0.80 mm \times 0.80 mm |

(1) For all available packages, see the orderable addendum at the end of the data sheet.

4 Simplified Schematic

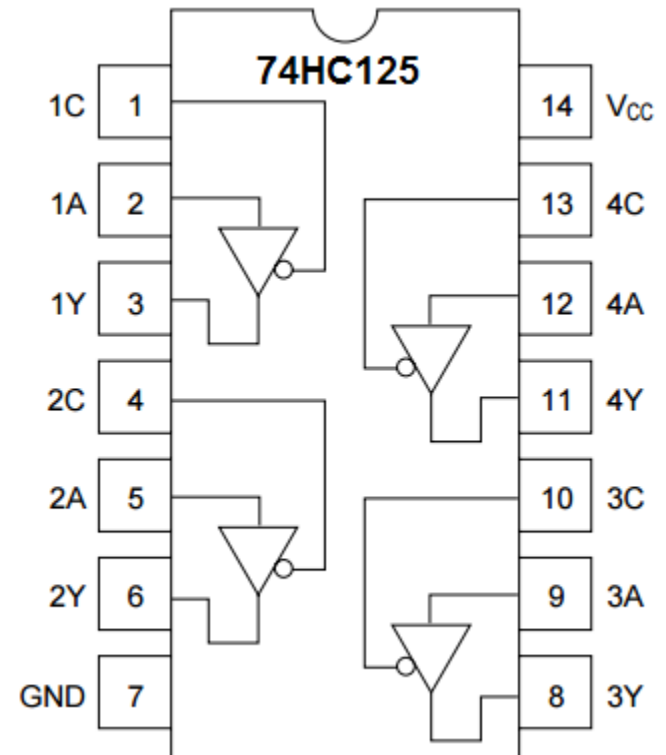 


LATCH AND BUFFER

Latch vs Buffer


- Buffers and Latches are different in concepts and usages.
- Latch is in a digital circuit for holding data until a clearing or enable signal send to the latch then the data will be changed.
- Latch is just to hold memory.
- Buffer uses both analog and digital signal
- Buffer is not just to hold memory but also to increase output power or changing output impedance.

Latch/buffer concept

 

Latch circuit functions

 
- Hold data from inputs
- Control the data holding with clock/enable pin
- Have an output enable pin to control on/off output signal



Buffer circuit functions


- No hold logic data
- Pass through by amplify the signal
- Some buffer has an enable pin to on/off output signal

Work of the buffer circuit

 


“Z” is a high-impedance state similarly no-connection state.

Work of the buffer circuit

 


“Z” is a high-impedance state similarly no-connection state.

Work of the buffer circuit

 


“Z” is a high-impedance state similarly no-connection state.

Work of the latch circuit

 


“Z” is a high-impedance state similarly no-connection state.

Work of the latch circuit

 


“Z” is a high-impedance state similarly no-connection state.

Work of the latch circuit

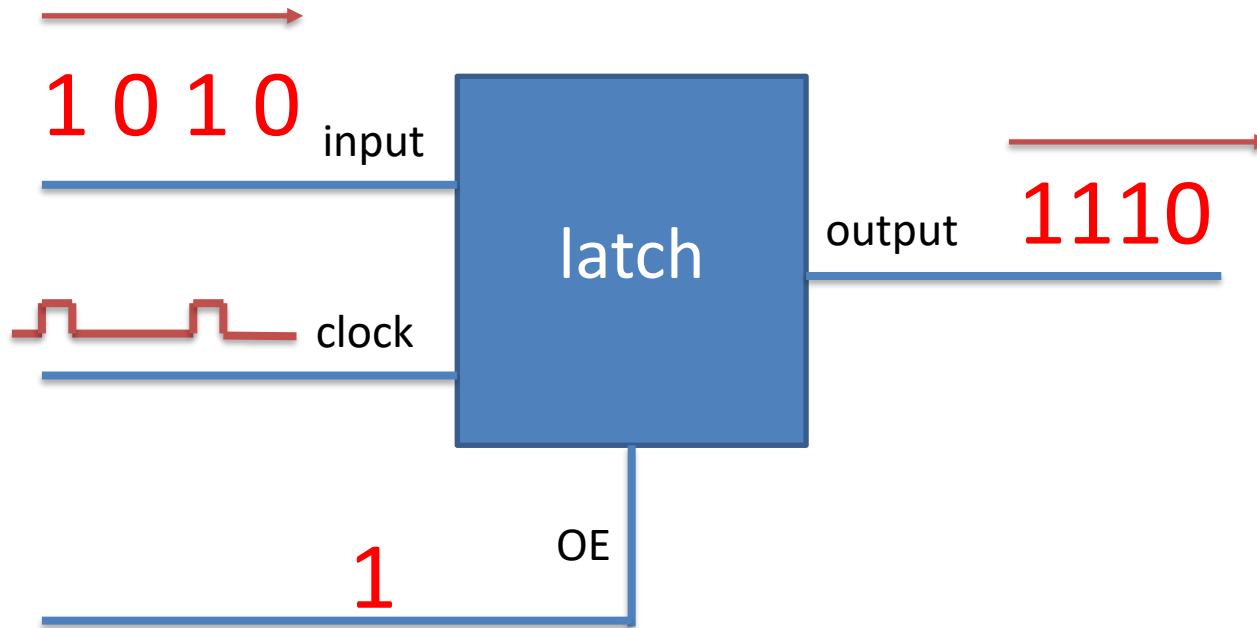


“Z” is a high-impedance state similarly no-connection state.

Latch/buffer in the computer

 


WWW.LEARNERSWINGS.COM

 

Buffer


WWW.LEARNERSWINGS.COM

Last Minute
ENGINEERS.com

 


SET-RESET FLIP-FLOP

SR Flip-Flop truth table

 

| S | R | Q | State |
|---|---|----------------|-----------|
| 0 | 0 | Previous state | No change |
| 0 | 1 | 0 | Reset |
| 1 | 0 | 1 | Set |
| 1 | 1 | ? | Forbidden |

SR Flip-flop analysis

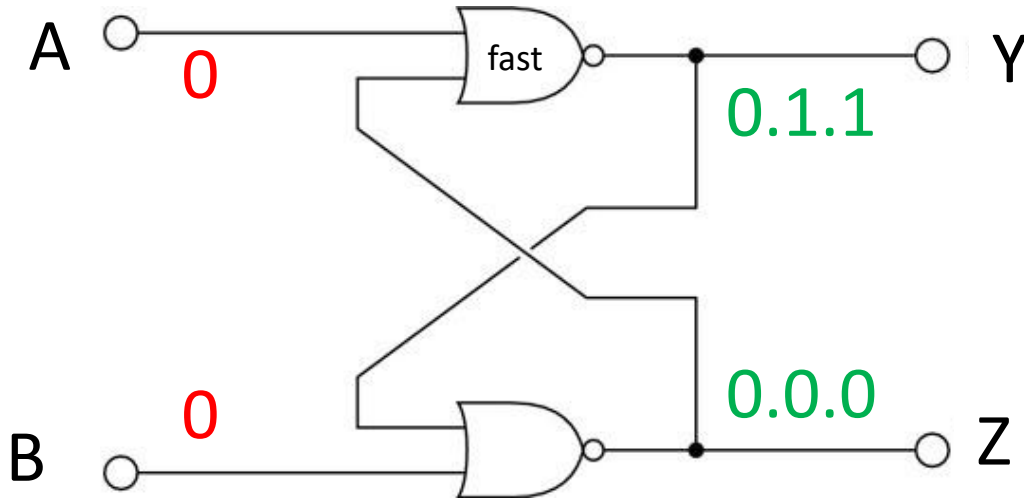


NOR
00 1
01 0
10 0
11 0

Step1

| A | B | Y | Z |
|---|---|---|---|
| 0 | 0 | 1 | 0 |
| 0 | 1 | | |
| 0 | 0 | | |
| 1 | 0 | | |
| 0 | 0 | | |
| 0 | 1 | | |

SR Flip-flop analysis

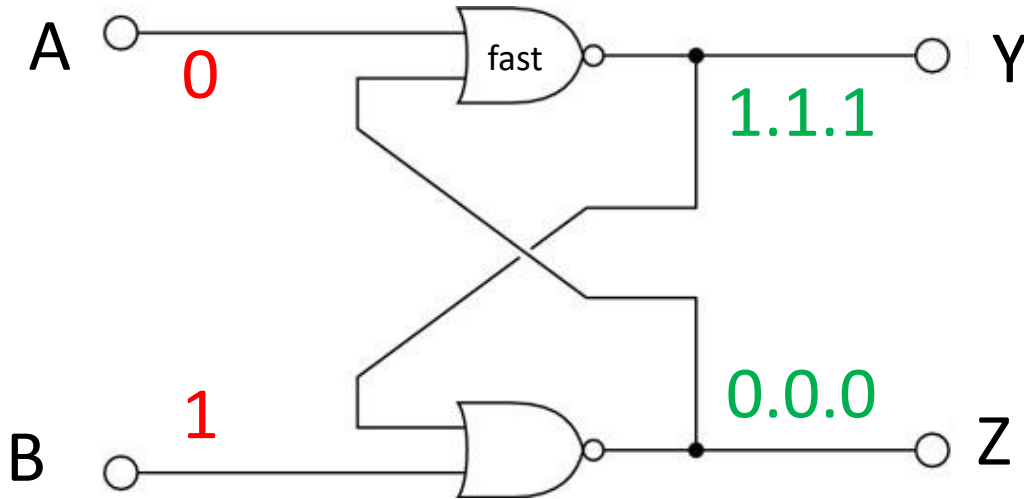


NOR
00 1
01 0
10 0
11 0

Step2

| A | B | Y | Z |
|---|---|---|---|
| 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 |
| 0 | 0 | | |
| 1 | 0 | | |
| 0 | 0 | | |
| 0 | 1 | | |

SR Flip-flop analysis

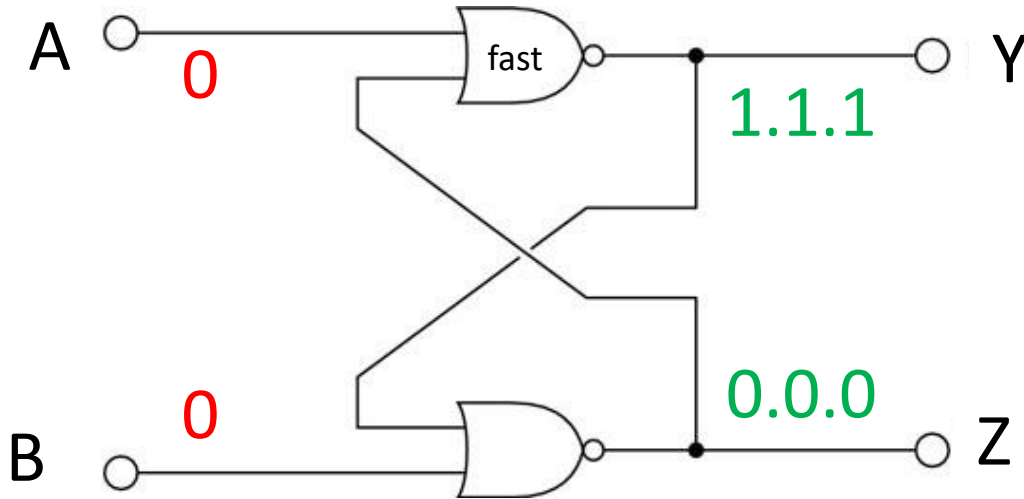


NOR
00 1
01 0
10 0
11 0

| A | B | Y | Z |
|---|---|---|---|
| 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 |
| 0 | 0 | 1 | 0 |
| 1 | 0 | | |
| 0 | 0 | | |
| 0 | 1 | | |

Step3

SR Flip-flop analysis

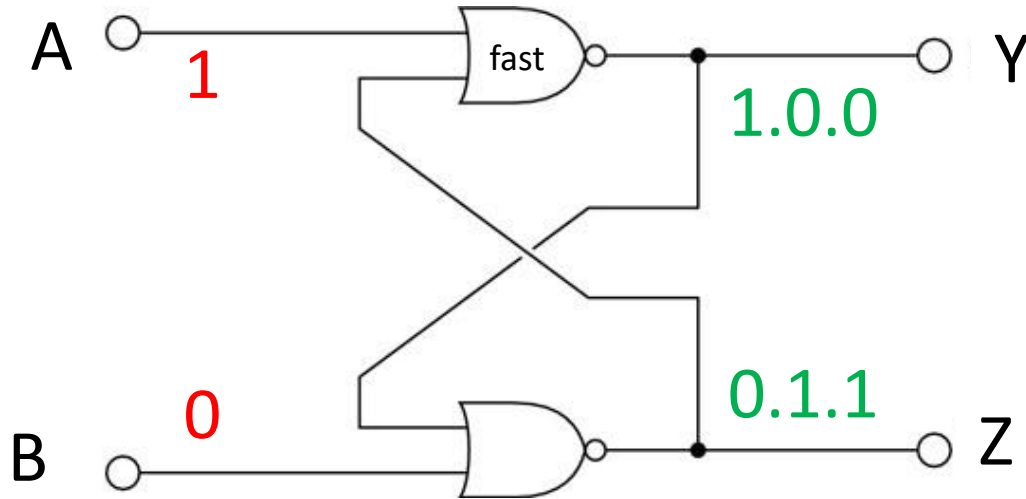


NOR
00 1
01 0
10 0
11 0

| A | B | Y | Z |
|---|---|---|---|
| 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 |
| 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 0 | 0 | | |
| 0 | 1 | | |

Step4

SR Flip-flop analysis

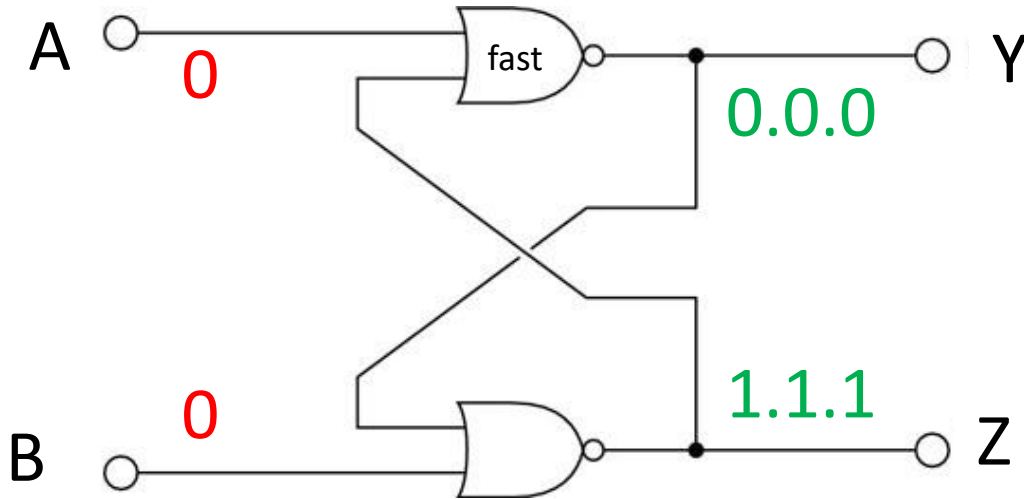


NOR
00 1
01 0
10 0
11 0

| A | B | Y | Z |
|---|---|---|---|
| 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 |
| 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 |
| 0 | 1 | | |



SR Flip-flop analysis

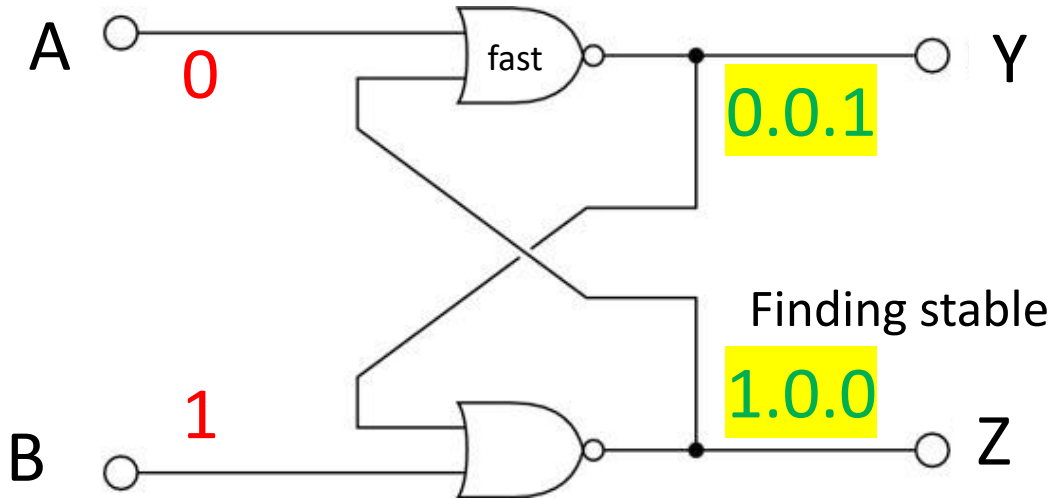


NOR
00 1
01 0
10 0
11 0

| A | B | Y | Z |
|---|---|---|---|
| 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 |
| 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 |

Step6


Truth table of SET/RESET – Flip Flop

 


NOR
00 1
01 0
10 0
11 0

| Reset | Set | Q | Q' | |
|-------|-----|---|----|-----------|
| 0 | 0 | 1 | 0 | |
| 0 | 1 | 1 | 0 | |
| 0 | 0 | 1 | 0 | No change |
| 1 | 0 | 0 | 1 | |
| 0 | 0 | 0 | 1 | No change |
| 0 | 1 | 1 | 0 | |

Activity 3.1 Build the SR flipflop on ThinkerCAD

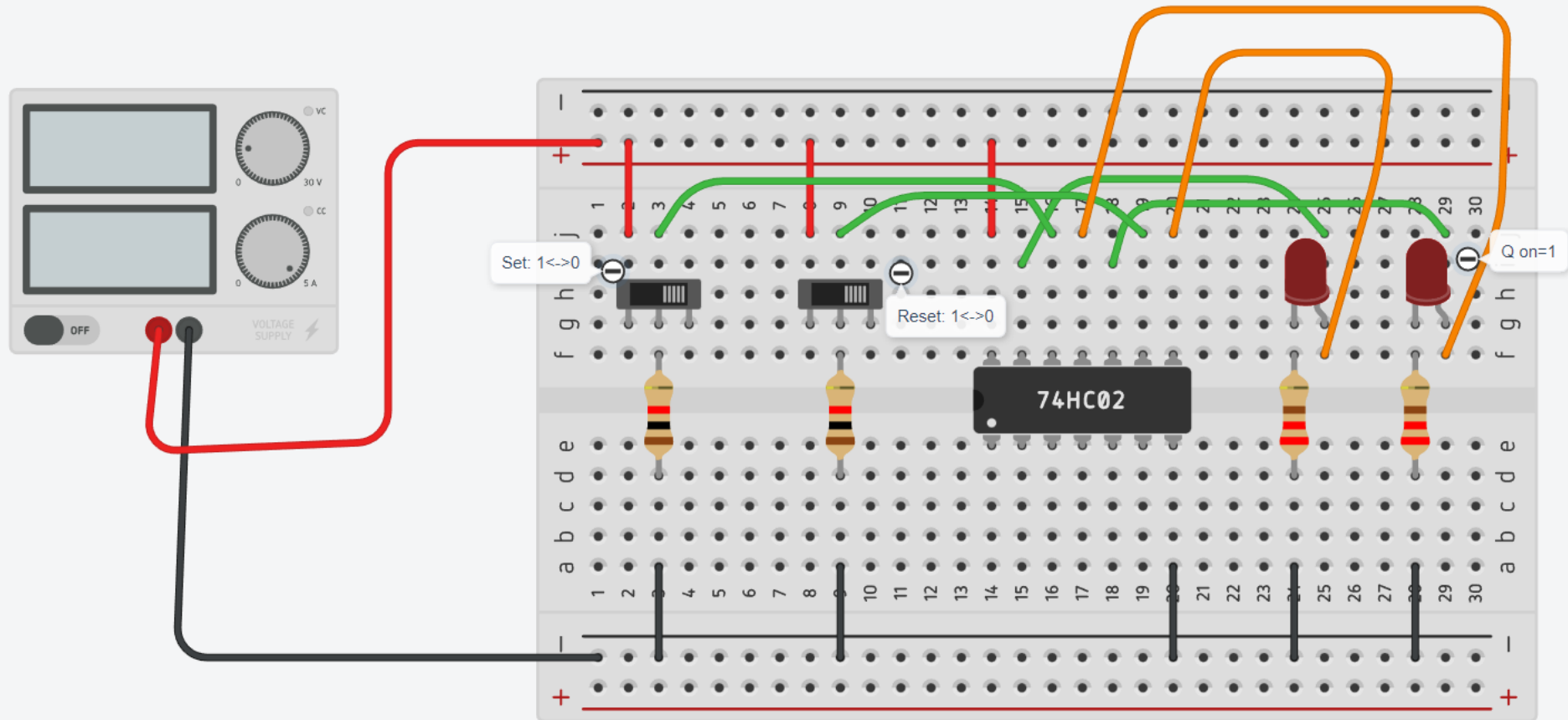

 Activity 3.2 Build the SR flipflop with clock on ThinkerCAD



Reference