

Chapter4: Counter and DAC & ADC Part-I

Asst.Prof.Dr.Supakit Nootyaskool



Objective

- Recognize type of flipflops and realize difference between rising edge/falling edge trigger.
- Clarify mechanism inside a counter circuit and express technique of counting up/down.
- Explain and illustrate concept of convert analog signal to digital signal.

Topic

- Combinational logic vs Sequential logic circuit
- Rising/Falling edge trigger
- JK-flipflop
- D-flipflop
- T-flipflop
- Frequency division circuit
- First-in first-out circuit
- Counter circuit
- Analog signal to Digital signal concept

COMBINATIONAL LOGIC CIRCUIT VS SEQUENTIAL LOGIC CIRCUIT

World of digital logic circuit

Combinational
logic circuit

Sequential
logic circuit

Key characteristics

Combinational logic circuit


- Memoryless
- Output instant in time
- No clock signal

Sequential logic circuit


- Memory
- Output depends on previous states
- Related clock signal

RISING AND FALLING EDGE TRIGGER


Rising/Falling edge trigger

 

 Flip-flop symbols in rising/falling edge trigger




Positive edge-triggered flip-flops

 


Negative edge-triggered flip-flops

Some textbook for rising/falling edge trigger called positive/negative edge trigger

Circuit detects positive edge trigger

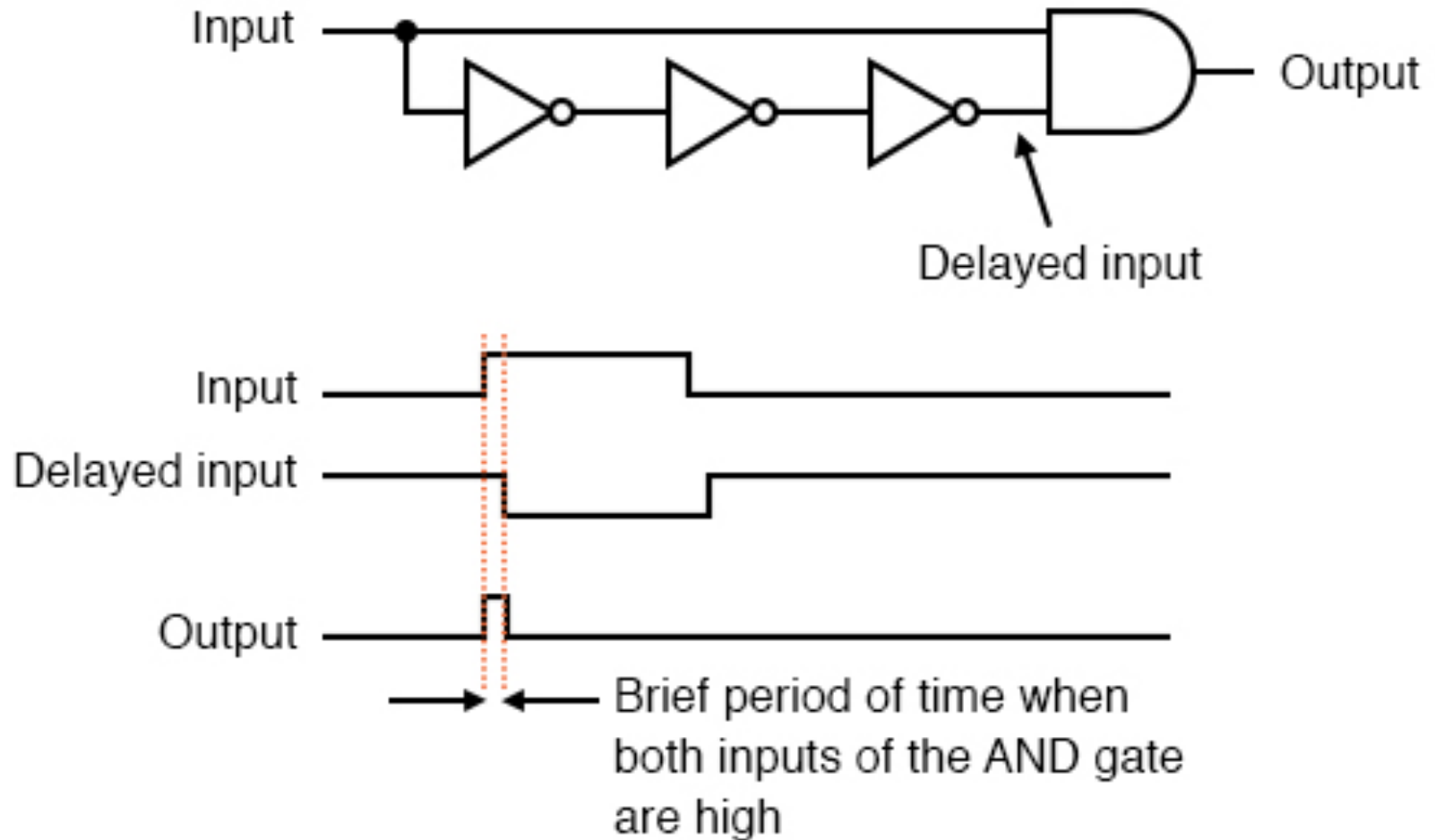

 
Activity 4.1 Delay time measurement in the positive-edge trigger circuit




SR FLIP-FLOP

Set-Reset Flip-flop (SR-flipflop)


 
SR flipflop is two types by the structure of logic gate.



NOR gate SR-flipflop

 


NAND gate SR-flipflop

  


Set-Reset Flip-flop (SR-flipflop)

Truth table

 


S	R	Q
0	0	No change
0	1	1 = Set
1	0	0 = Reset
1	1	Restrict Combination

NOR gate SR-flipflop

 


Example application uses SR-flipflop

- Debounced switch

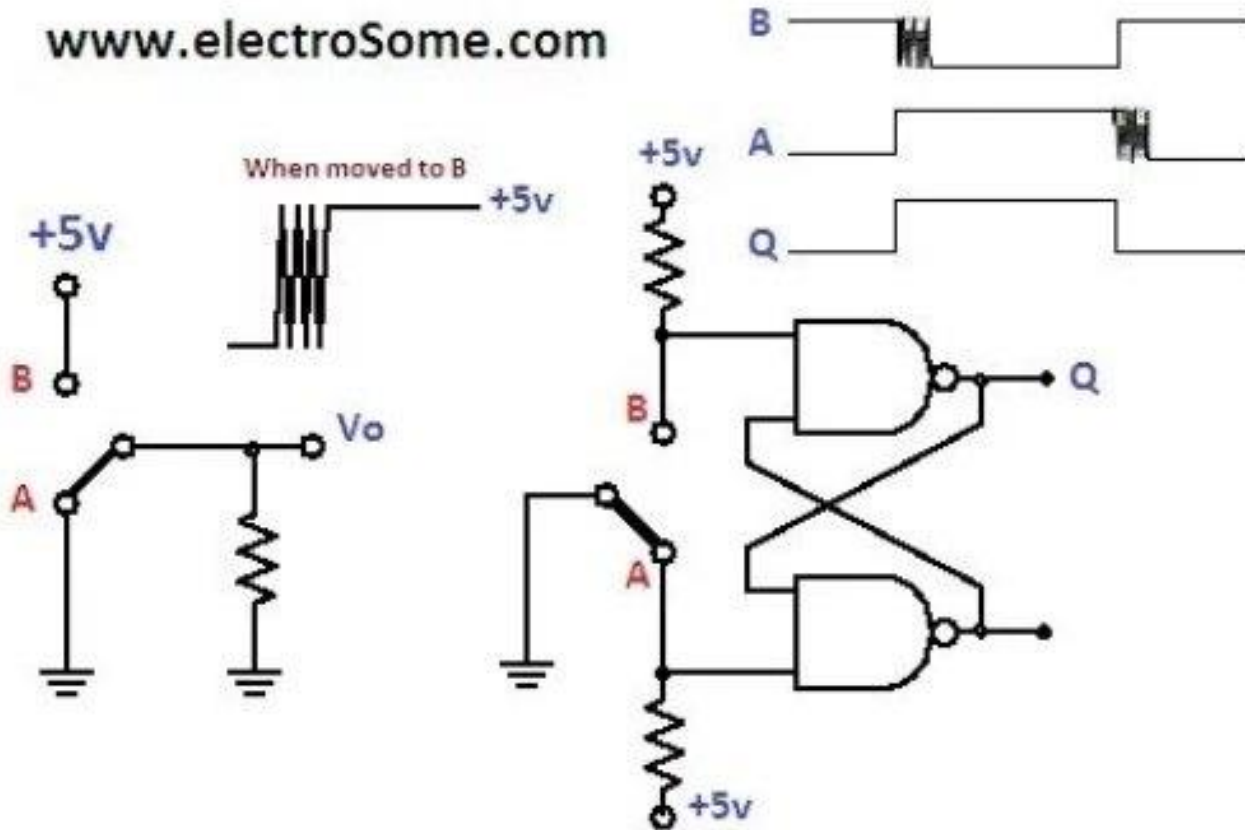


JK FLIP-FLOP

JK Flip-flop

 


 - Invented by Jack Kilby
- The JK flip-flop modified from SR flip-flop by adding a clock input to prevent the invalid output condition that occurs when both S and R are equal to logic "1".





Switching Example: J-K Flip-Flop

 


The positive going transition (PGT) of the clock enables the switching of the output Q. The "enable" condition does not persist through the entire positive phase of the clock. The J & K inputs alone cannot cause a transition, but their values at the time of the PGT determine the output according to the [truth table](#). This is an application of the versatile [J-K flip-flop](#).




JK Flip-flop Truth table

Clk	J	K	Q	Description
No clock	?	?	?	No change
	0	0	?	No change
	0	1	?->0	Reset
	1	0	?->1	Set
	1	1	0->1 1->0	Toggle

JK flip-flop in timing states

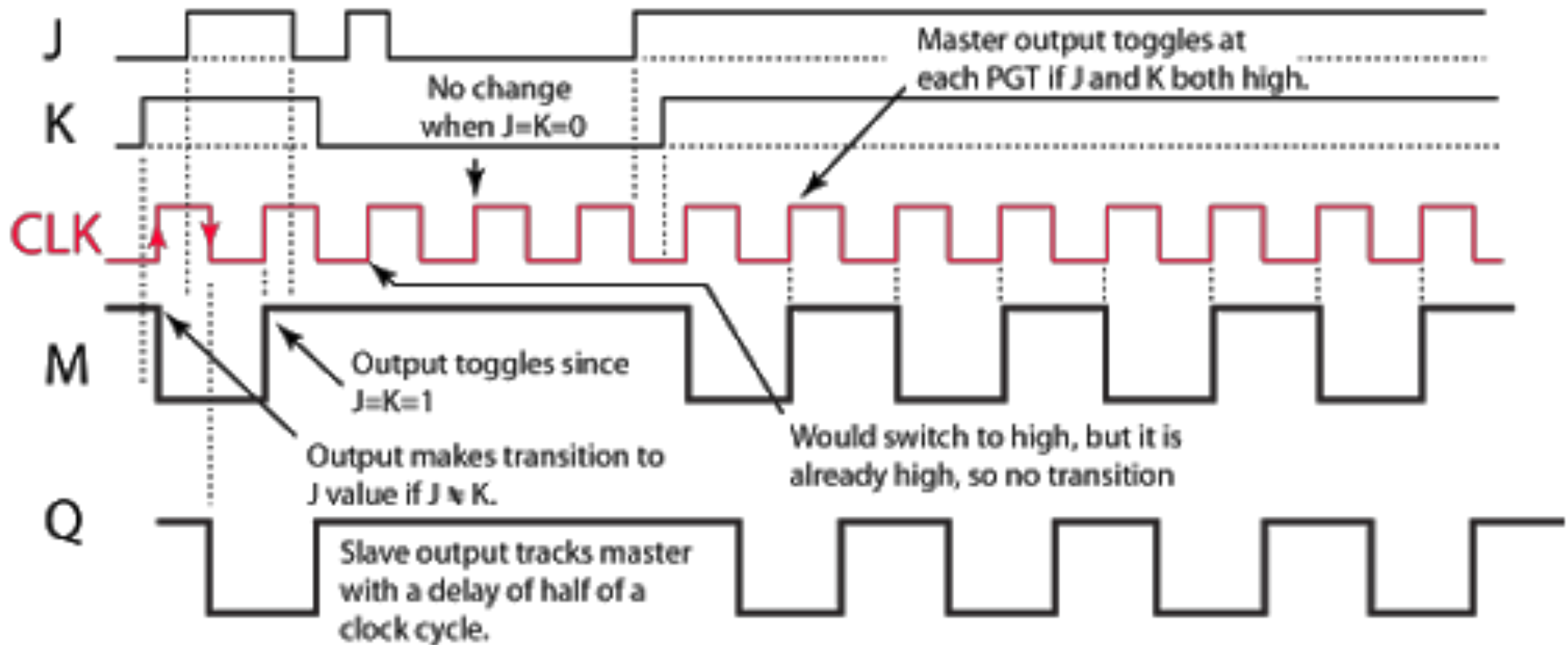


 

Application used JK flip-flop





D FLIP-FLOP AND T FLIP-FLOP

 
Making D flip-flop from JK



Clk	J	K	Q	Description
No clock	?	?	?	No change
	0	1	?->0	Store "0"
	1	0	?->1	Store "1"


T Flip-flop from D and JK

  

Clk (T)	Q	Description
No clock	?	No change
	?->0 ?->1	Toggle


4-BIT LATCH CIRCUIT

4-bit Latch circuit

 


FREQUENCY DIVISION CIRCUIT

Frequency division circuit

 

4-BIT FIFO CIRCUIT

4-bit First-in First-out (FIFO)

 

COUNTER



Counter circuit


- The digital circuit has divided type of counter circuit by focusing at a characteristic of input clock to the gate in the circuit.

Asynchronous
circuit


Synchronous
circuit

Asynchronous counter

  

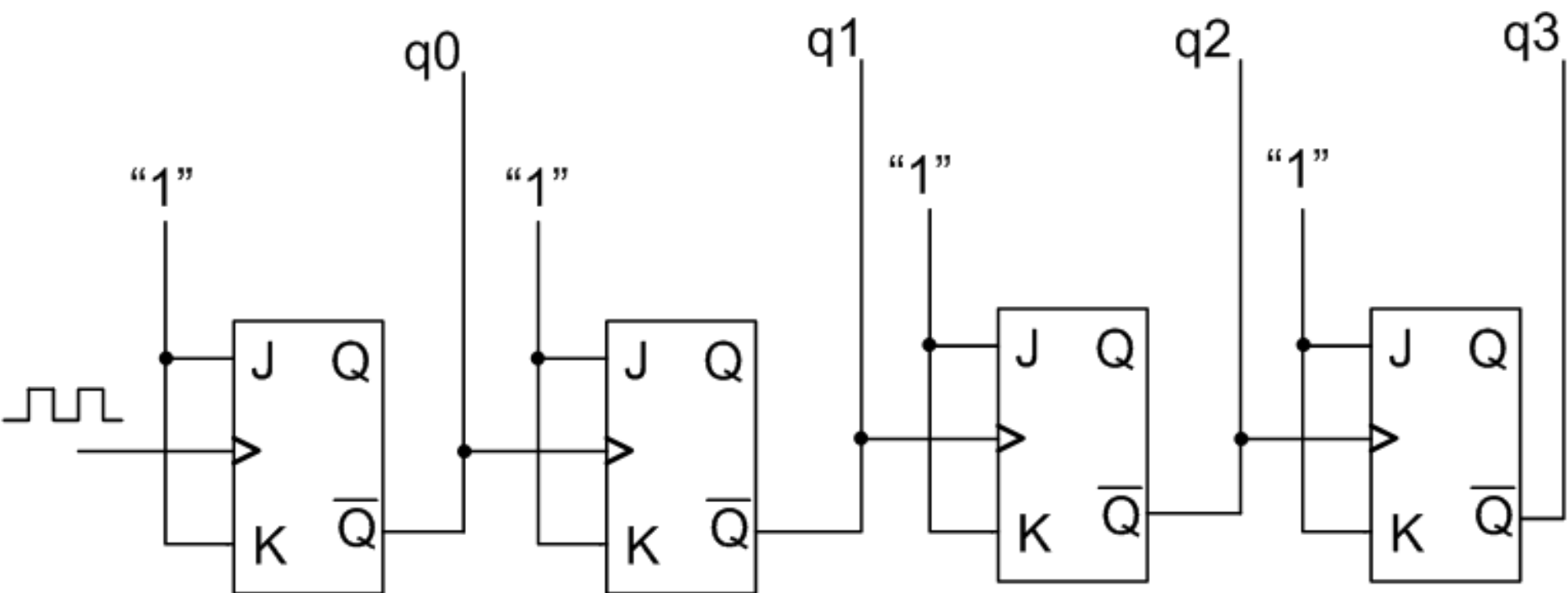

2-bit Asynchronous count up/down circuit

 




Delay-time problem in asynchronous counter circuit



**SN5404, SN54LS04, SN54S04,
SN7404, SN74LS04, SN74S04
HEX INVERTERS**

SDLS029C - DECEMBER 1983 - REVISED JANUARY 2004

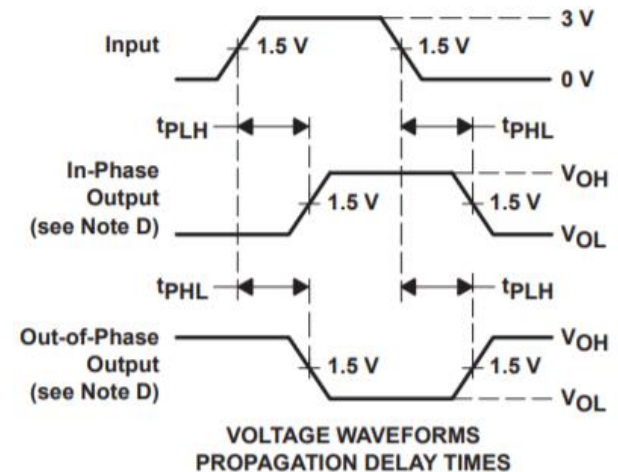  SN5404 . . . J PACKAGE
SN54LS04, SN54S04 . . . J OR W PACKAGE
SN7404, SN74LS04 . . . D, N, OR NS PACKAGE
SN74LS04 . . . D, DB, N, OR NS PACKAGE
(TOP VIEW)




switching characteristics, $V_{CC} = 5\text{ V}$, $T_A = 25^\circ\text{C}$ (see Figure 1)

PARAMETER	FROM (INPUT)	TO (OUTPUT)	TEST CONDITIONS	SN54S04 SN74S04			UNIT
				MIN	TYP	MAX	
t_{PLH}	A	Y	$R_L = 280\ \Omega$, $C_L = 15\text{ pF}$		3	4.5	ns
t_{PHL}					3	5	

Asynchronous counter issue




(TOP VIEW)

 

'76
FUNCTION TABLE


INPUTS					OUTPUTS	
PRE	CLR	CLK	J	K	Q	\bar{Q}
L	H	X	X	X	H	L
H	L	X	X	X	L	H
L	L	X	X	X	H [†]	H [†]
H	H		L	L	Q ₀	\bar{Q}_0
H	H		H	L	H	L
H	H		L	H	L	H
H	H		H	H	TOGGLE	

 


switching characteristics, $V_{CC} = 5\text{ V}$, $T_A = 25^\circ\text{C}$ (see note 3)

PARAMETER	FROM (INPUT)	TO (OUTPUT)	TEST CONDITIONS	MIN	TYP	MAX	UNIT
f _{max}			R _L = 2 kΩ, C _L = 15 pF	30	45		MHz
t _{PLH}	PRE, CLR or CLK	Q or Q̄			15	20	ns
t _{PHL}					15	20	ns

Asynchronous vs Synchronous counter

 


 - Clock or control signal getting from previous states
- Easy design the counter circuit.
- Not suitable for a critical time system.



- A clock signal controls all states
- Complexity for design counter circuit.
- Proper for the critical time system

Example 3-bit synchronous counter-up

 

ลำดับ ck	Q2	Q1	Q0	อธิบาย
1	0	0	0	นับ 0
2	0	0	1	นับ 1
3	0	1	0	นับ 2
4	0	1	1	นับ 3 เอา q0 and q1 = 1
5	1	0	0	นับ 4 เกิด toggle ที่ q2
6	1	0	1	นับ 5
7	1	1	0	นับ 6
8	1	1	1	นับ 7 เอา q0 and q1 = 1
9	0	0	0	นับ 0 เกิด toggle ที่ q2

ANALOG SIGNAL AND DIGITAL SIGNAL

Analog signal vs Digital signal

Analog Signal



Digital Signal




Analog signal vs Digital signal


Analog Signal



 
Analog signals are continuous-time signals changing the wave from continuously.



 
Digital signals are discrete-time signals limited by number of **bits** and the **sampling rate**.




Digital Signal

 


Signal Property

 


Which one is the low frequency?

 


Which one is the low frequency?

 


Activity 4.2 Frequency calculation

 

Amplitude, Voltage, Level

 

Modulation

 

A

+


B

=

C


Activity 4.3 AM Simulation with Excel

A		B		C
0.314159	0.309017	0.628319	0.587785	0.896802
0.628319	0.587785	1.256637	0.951057	1.538842
0.942478	0.809017	1.884956	0.951057	1.760074
1.256637	0.951057	2.513274	0.587785	1.538842
1.570796	1	3.141593	1.23E-16	1
1.884956	0.951057	3.769911	-0.58779	0.363271
2.199115	0.809017	4.39823	-0.95106	-0.14204
2.513274	0.587785	5.026548	-0.95106	-0.36327
2.827433	0.309017	5.654867	-0.58779	-0.27877
3.141593	1.23E-16	6.283185	-2.5E-16	-1.2E-16
3.455752	-0.30902	6.911504	0.587785	0.278768
3.769911	-0.58779	7.539822	0.951057	0.363271
4.08407	-0.80902	8.168141	0.951057	0.14204
4.39823	-0.95106	8.796459	0.587785	-0.36327
4.712389	-1	9.424778	3.68E-16	-1
5.026548	-0.95106	10.0531	-0.58779	-1.53884
5.340708	-0.80902	10.68142	-0.95106	-1.76007
5.654867	-0.58779	11.30973	-0.95106	-1.53884
5.969026	-0.30902	11.93805	-0.58779	-0.8968
6.283185	-2.5E-16	12.56637	-4.9E-16	-7.4E-16
6.597345	0.309017	13.19469	0.587785	0.896802
6.911504	0.587785	13.82301	0.951057	1.538842
7.225663	0.809017	14.45133	0.951057	1.760074
7.539822	0.951057	15.07964	0.587785	1.538842
7.853982	1	15.70796	6.13E-16	1
8.168141	0.951057	16.33628	-0.58779	0.363271
8.4823	0.809017	16.9646	-0.95106	-0.14204
8.796459	0.587785	17.59292	-0.95106	-0.36327
9.110619	0.309017	18.22124	-0.58779	-0.27877
9.424778	3.68E-16	18.84956	-7.4E-16	-3.7E-16
9.738937	-0.30902	19.47787	0.587785	0.278768
10.0531	-0.58779	20.10619	0.951057	0.363271
10.36726	-0.80902	20.73451	0.951057	0.14204
10.68142	-0.95106	21.36283	0.587785	-0.36327
10.99557	-1	21.99115	8.58E-16	-1

 

Convert Analog Signal to Digital Signal


- Step1: Analog signal

 

Convert Analog Signal to Digital Signal

- Step2: Define the number of levels (bits)


Suppose: 4 levels

 

Convert Analog Signal to Digital Signal

- Step3: Define the number of sampling


Suppose: 5 samples / 1 cycle

 

Convert Analog Signal to Digital Signal


- Step4: Map the level and sampling to the signal

Suppose: 5 samples / 1 cycle

 


Convert Analog Signal to Digital Signal

- Step5: Reading digital signal

 

 Activity 4.4 Drawing 8 levels and 10 sampling



Reference

- <https://www.quora.com/What-is-an-application-of-an-RS-flip-flop>
- <https://electronics.stackexchange.com/questions/jk-flip-flop-toggle>